

Student Name: Noe Romeo

CS 4341 Homework 1 – Class Section 002/003 (please circle one)
Dr. Doug DeGroot's Class


Instructions:

1. This homework is due on Thursday, September 17.
2. Please print and use a copy of this handout for your answers. You may add extra pages as needed. When you're done, scan all pages and group them into a single PDF file (no Word Text files or anything else; only PDF).
3. Draw and write neatly and legibly. If neither I nor our graders can read your answers, points will be deducted for the entire question.
4. Show all work, including intermediate calculations. Add simple explanations for each step where appropriate.
5. On each circuit diagram, label all inputs and outputs.
6. Use alphabetic ordering of variables when writing Boolean expressions, and use standard binary number order for your Truth Tables.
7. For each mistake in your answers, diagrams, tables, etc., a minimum of 2-4 points will be deducted. Totally wrong final answers will have all points for that question deducted.
8. Sign your name to the top sheet of your papers.
9. Do all work on your own, but you may use the book, web, etc., just not each other.

1. Are any of the following pairs of circuits equivalent? Circle the correct answer. 10 pts!

A	B	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$	$\bar{A} + \bar{B}'$	AB	\bar{AB}	\bar{AB}'
0	0	1	1	0	0	0	1	0
0	1	1	0	1	1	0	0	1
1	0	0	1	1	0	1	0	0
1	1	0	0	0	1	1	0	1

$A+B$	$\bar{A} + \bar{B}$	$A\bar{B}$	\bar{AB}
0	1	0	1
1	0	1	0
0	0	0	0
1	1	0	1

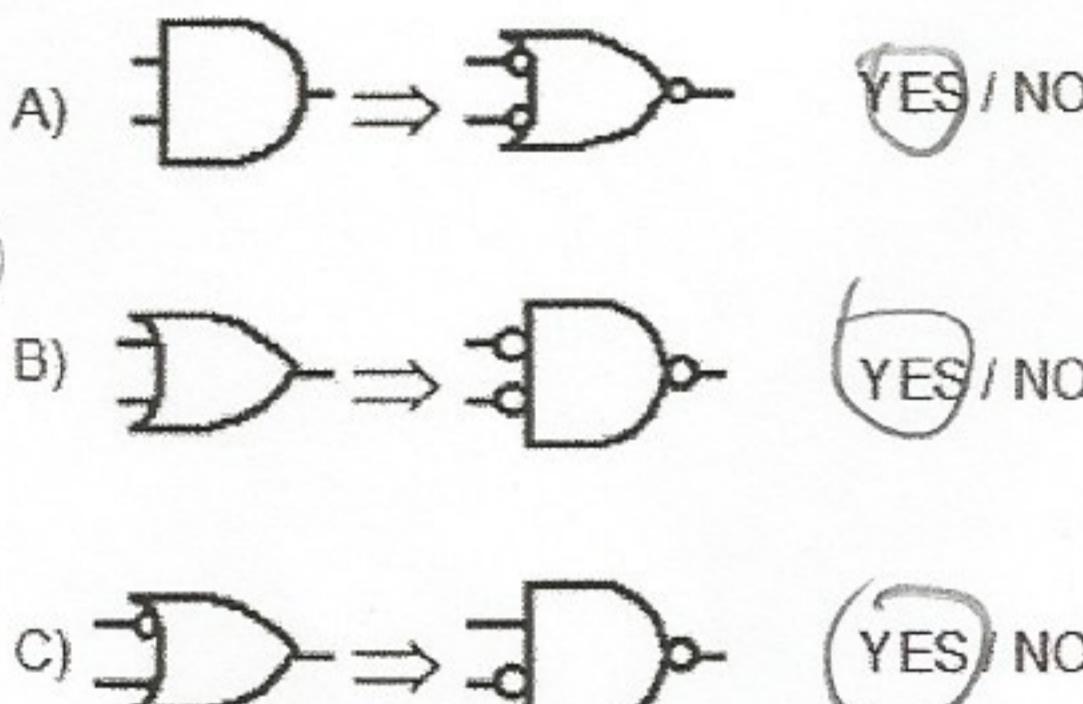

2. Determine whether the following function is true or false. Show/explain your reasoning. 10 pts!

$$\text{eq 1: } x'y' + x'z + x'z' = \text{eq 2: } x'z' + y'z' + x'z$$

True: _____

False: FAKE

$$\text{let eq1} = x'y + x'z + x'z' \quad 10 \text{ pts}$$

$$\text{let eq2} = x'z' + y'z' + x'z$$

eq1 \neq eq2

since eq1 $\Rightarrow x'y'$

& eq2 $\Rightarrow x' + y'z'$

eq2 output depends

on three variables

& eq1 output depends

on only two variables

$$\begin{aligned} \text{eq 1} \\ x'y' + x'z + x'z' \\ x'(y' + z + z') \end{aligned}$$

$$x'(y' + 1) \rightarrow y' + 1 = y'$$

$$x'y'$$

$$\begin{aligned} \text{eq 2} \\ x'z' + y'z' + x'z \\ x'(z' + z) + y'z' \\ x' + y'z' \end{aligned}$$

#3 Note full work & final answers for number 3 can be found in the following page

3. Write the following expression in both minimal and canonical Sum of Products (SOP) form.

10 pts

m ₁	x	v	v	x	x	a	b	c	d
m ₂	x	v	v	x	x	a	b	c	d
m ₃	x	v	x	x	v	a	b	c	d
m ₄	x	v	x	x	v	a	b	c	d
m ₅	x	x	v	v	v	a	b	c	d

$$(b+d)(a'+b'+c) = b\bar{a}^2 + b\bar{b}' + \bar{b}c + d\bar{c}' + db\bar{b}' + d\bar{c}$$

$$= b\bar{b}(a' + 1 + c) + d(a' + b' + c)$$

$$= b(\bar{a}^2 + c) + d(a' + b' + c)$$

$$= \bar{b}\bar{a}^2 + bc + da' + db' + dc$$

Minimal: $\bar{b}\bar{a}^2 + bc + da' + db' + dc$

$$m_1 m_2 m_3 m_4 m_5$$

$$\bar{b}\bar{a}^2 + bc + da' + db' + dc$$

Canonical: $\bar{a}^2\bar{b}cd + \bar{a}^2\bar{b}c\bar{d}' + \bar{a}^2\bar{b}\bar{c}d + \bar{a}^2\bar{b}\bar{c}\bar{d}' + abc\bar{d} + ab\bar{c}\bar{d}' + ab\bar{c}d + ab\bar{c}\bar{d}' + ab\bar{c}d + ab\bar{c}\bar{d}'$

$$\bar{b}\bar{c}^2(c+\bar{c})(d+d') + (\bar{b}c(c+a))(d+d') + da(b+b')(c+\bar{c}) + db(c+a')(c+\bar{c}) + dc(c+a')(b+b')$$

$$(b\bar{a}^2(c+\bar{b}\bar{c}^2)(d+d')) (b\bar{c}a + b\bar{c}\bar{a})(d+d')$$

$$\cancel{db\bar{a}^2c + d'\bar{b}a^2c + d'\bar{b}\bar{a}^2c + d'\bar{b}\bar{c}^2} + \cancel{db\bar{c}a + d'\bar{b}\bar{c}a + d'\bar{b}\bar{c}\bar{a}}$$

#4 Note the full work for finding the minimal equation can be found in the following papers

4. Write the following expression in both minimal and canonical Product of Sums (POS) form.

10 pts

$$\bar{a}^2b(c+\bar{c}) + \bar{a}'\bar{c}(b'+\bar{b}) + a'b\bar{c}$$

$$\bar{a}'b\bar{c} + a'b\bar{c} + a'\bar{c}\bar{b}' + \bar{a}\bar{c}\bar{b} + \bar{a}\bar{b}\bar{c}$$

Minimal: $\bar{a}^2b(c+\bar{c}) + a'b\bar{c}$

$$\begin{matrix} a'b(1+c) \\ \bar{a}'b\bar{c} \end{matrix}$$

$$let. y = a^2b + a^2\bar{c} + ab\bar{c}$$

Canonical: $(\bar{a} + b + \bar{c})(a + b + \bar{c})(a + \bar{b} + \bar{c})(\bar{a} + \bar{b} + c)$

a	b	c	a'	c'	$\bar{a}b$	$a'c'$	abc	$\bar{a}'b + a'c' + abc$	Maxterm	
									$\bar{a} + b + \bar{c}$	$\bar{a} + \bar{b} + \bar{c}$
1	0	1	0	0	0	0	0	0	$\bar{a} + b + \bar{c}$	$\bar{a} + \bar{b} + \bar{c}$
1	1	1	0	0	1	0	1	1	$\bar{a} + \bar{b} + \bar{c}$	$\bar{a} + b + \bar{c}$
0	0	1	1	0	0	0	0	0	$a + b + \bar{c}$	$a + \bar{b} + \bar{c}$
0	1	1	1	0	0	0	0	0	$a + \bar{b} + \bar{c}$	$a + b + \bar{c}$
1	0	0	0	1	0	0	0	0	$\bar{a} + b + \bar{c}$	$\bar{a} + \bar{b} + \bar{c}$
1	1	0	0	1	1	0	0	1	$\bar{a} + \bar{b} + \bar{c}$	$\bar{a} + b + c$
0	0	0	1	1	0	1	0	1	$a + b + \bar{c}$	$a + \bar{b} + c$
0	1	0	1	1	0	1	0	1	$a + \bar{b} + c$	$a + b + c$

$$Y = (\bar{a} + b + \bar{c})(a + b + \bar{c})(a + \bar{b} + \bar{c})$$

$$(\bar{a} + \bar{b} + c)$$

#3

卷之六

卷之三

1200-2000 m

卷之三

W 5 - 6 C P

mark b)

my a' bid

1988

~~March 29, 1926~~

卷之三

卷之三

4. Part A ~ finding minimal

$$\begin{aligned} & \cancel{a'b(c+c')} + \cancel{a'c(b'+b)} + \cancel{abc} \\ & \cancel{b'c} + \cancel{a'b'} + \cancel{a'b} + \cancel{a'b} + abc \\ & \cancel{a'c(b+b')} + \cancel{bc(a'+c)} \\ & \underline{\cancel{a'c} + \cancel{bc}} \end{aligned}$$

4. Part B ~ finding maximal

$$a'c + b'b + b'c + bc$$

5. Obtain the truth tables of the following functions, and express each function in sum-of-products (SOP) form.

15 pts

				$y = (c' + d)(b + c')$	$y = (c+d)(b+c')$	Minterm	Minterm	\therefore
c	b	d	c'	$c+d$	$b+c'$	$c'd$	m_0	$\text{Let } y = F(c, b, d) = (c+d)(b+c')$
0	1	1	1	1	1	$\bar{c}d$	m_1	$y = (b\bar{c}d) + (bcd) + (\bar{b}\bar{c}\bar{d})$
1	0	1	0	1	1	$\bar{c}\bar{d}$	m_2	$+ (b\bar{c}\bar{d}) + (\bar{b}\bar{c}\bar{d})$
0	0	1	1	0	0	$\bar{c}b\bar{d}$	m_3	
1	0	0	1	1	0	$\bar{c}b\bar{c}$	m_4	
0	1	0	0	1	0	$\bar{c}b\bar{d}$	m_5	
1	1	0	0	1	1	$\bar{c}b\bar{d}$	m_6	
0	0	0	1	0	0	$c\bar{b}\bar{d}$	m_7	
1	0	0	0	0	0			

$$\text{Let } y = F(c, b, d) = (c+d)(b+c')$$

$$y = (b\bar{c}d) + (bcd) + (\bar{b}\bar{c}\bar{d}) + (b\bar{c}\bar{d}) + (\bar{b}\bar{c}\bar{d})$$

$$\text{Let } y = F(a, b, d) = (cd + b'c + bd')(b+d)$$

				$y = (cd + b'c + bd')(b + d)$	$y = (c+d+b'c+bd')(b+d)$	Minterm	$y = bcd + \bar{b}cd + \bar{b}\bar{c}d + b\bar{c}d$				
c	b	d	b'	cd	$b'c$	bd'	$c+d+b'c+bd'$	$b+d$	$(c+d+b'c+bd')(b+d)$		
1	1	1	0	0	1	0	0	1	1	1	$cb\bar{d}v$
1	0	1	1	0	1	0	1	1	1	1	$c\bar{b}d\bar{v}$
0	1	1	0	0	0	0	0	0	0	0	$\bar{c}\bar{b}d\bar{x}$
0	0	1	0	0	1	0	1	1	1	1	$\bar{c}\bar{b}d\bar{v}$
1	1	0	0	1	0	0	1	1	1	1	$cb\bar{d}v$
1	0	0	1	0	1	0	0	0	0	0	$c\bar{b}\bar{d}\bar{x}$
0	1	0	0	1	0	1	1	0	0	0	$\bar{c}\bar{b}\bar{d}\bar{v}$
0	0	0	1	0	0	0	0	0	0	0	$\bar{c}\bar{b}\bar{d}\bar{x}$

6. Given a functional specification in either a circuit, Boolean equation, or Truth Table, why would we want to simplify it if our simplified version is logically equivalent? 10 pts

We would want to use the simplified version so that we can decrease complexity & decrease cost when building a circuit.

7. Convert the following minimal Boolean formula to the correct canonical Sum-of-Products (SOP) form. Show your work.

3 vars a, b, c 10 pts

$$y = \overline{a} + b'c$$

$$m_1 \sim v \quad m_2 \sim x \\ Bx \quad cx \quad b'v \\ c'v$$

$$Y = a \cdot (b'+b)(c'+c) + (a^2+a)b'c$$

$$(c'b' + ab)(c' + c) + ab'c + ab'c$$

$$c'a'b' + (ab') + (ab + ab) + a'b'c + \cancel{abc}$$


$$Y = \overline{c} \overline{a} \overline{b}' + \overline{c} a b' + \overline{c} a b + c a b + c \overline{a} b'$$

$$Y = a b' c + a b' c' + a b c' + a b c + a^2 b' c$$

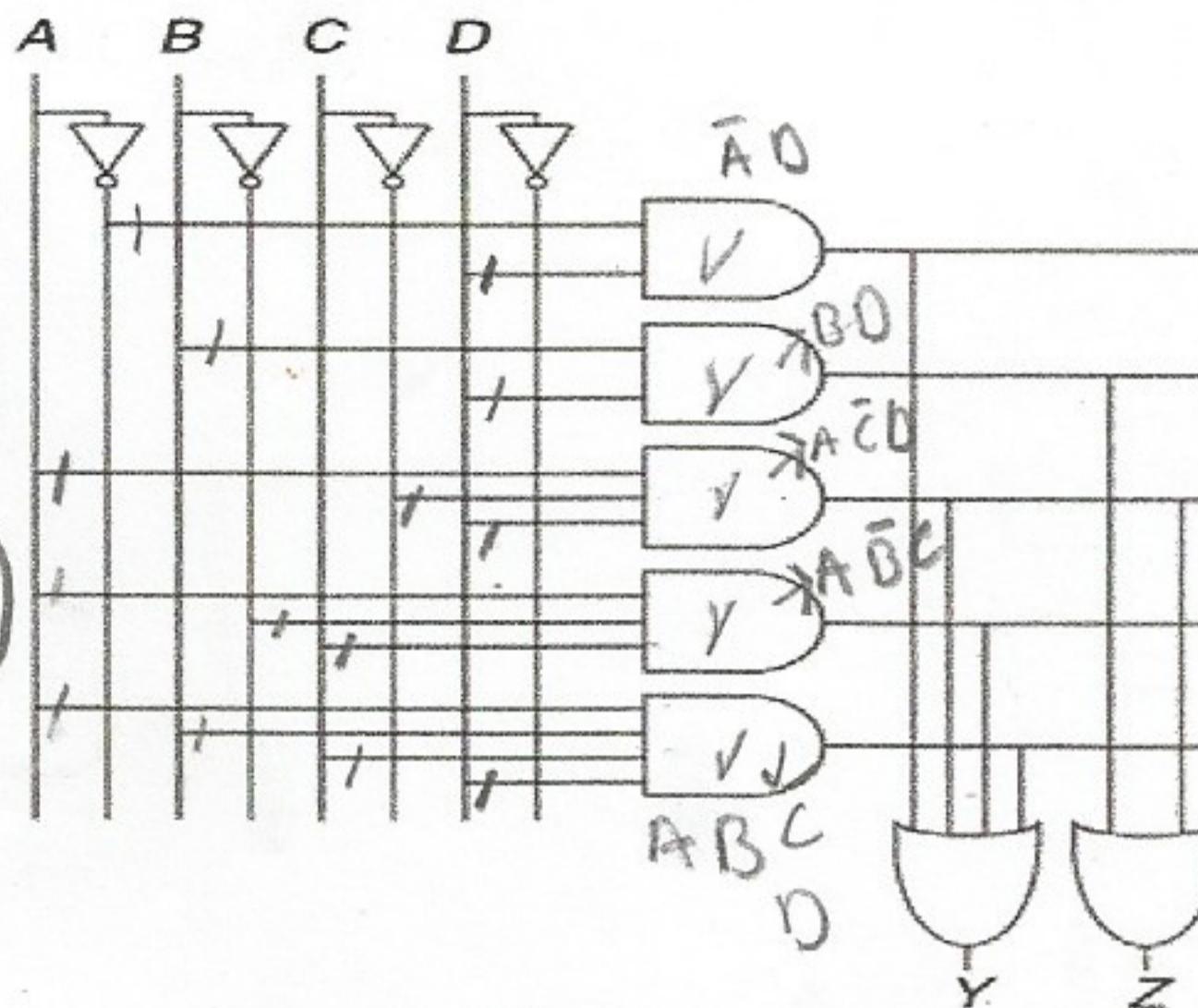8. Write Boolean equations for the outputs of the following circuit. Then minimize the equations using Boolean algebra manipulation. And then finally draw an improved circuit with the same function.


25 pts

$$\begin{aligned}
 Y &= \bar{A}D + A\bar{C}D + A\bar{B}C + ABCD \\
 &= D(\bar{A} + A\bar{C}) + AC(\bar{B} + BD) \\
 &= D(\bar{A} + \bar{C}) + ACC(\bar{B} + D) \\
 Y &= \bar{A}D + A\bar{C}D + ACC(\bar{B} + D) \\
 &\quad + D\bar{C}BA
 \end{aligned}$$



$$Z = BD + A\bar{D}\bar{C}$$

$$Z = D(B\bar{C} + A\bar{C})$$

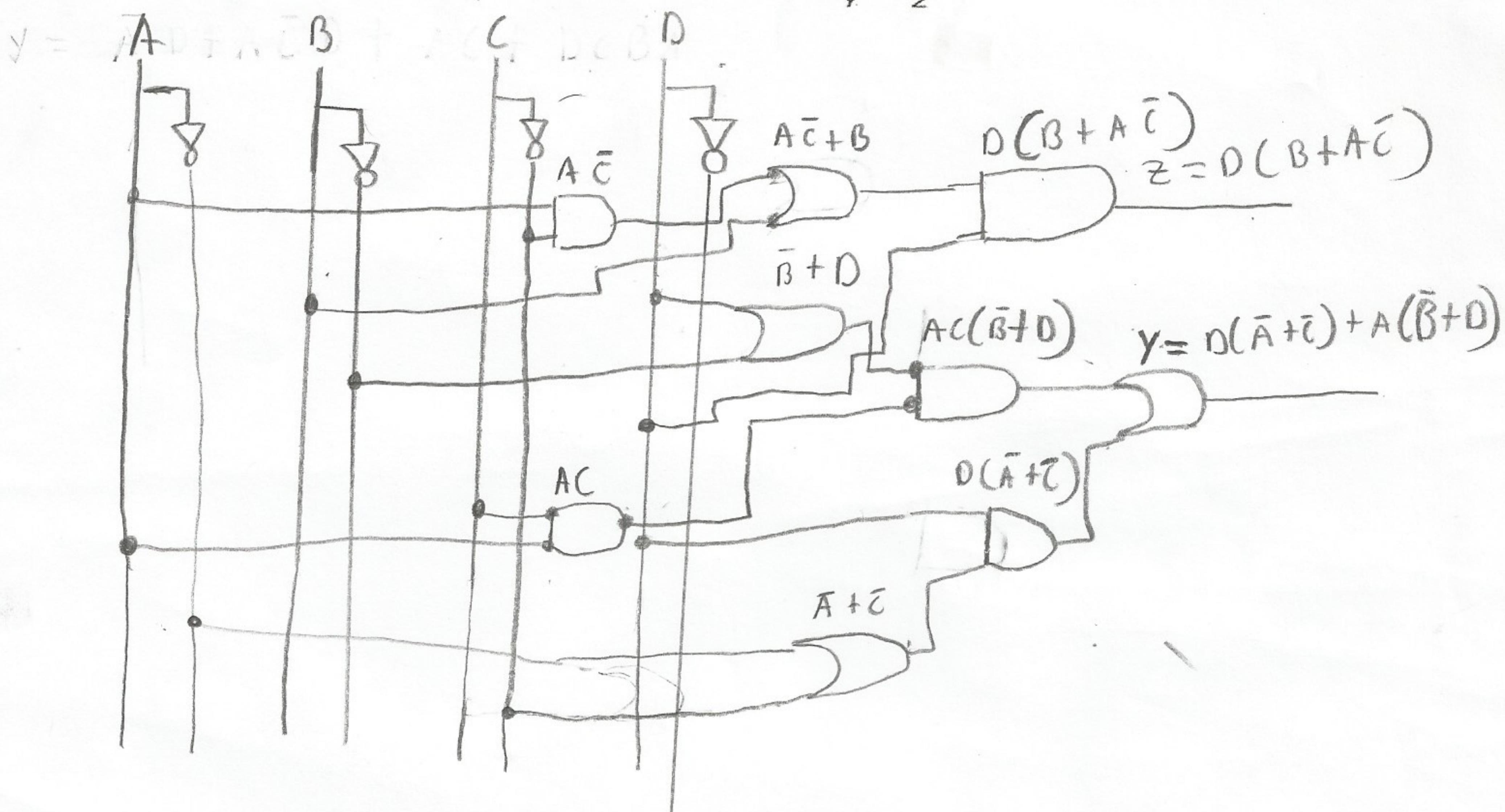

I did this homework entirely on my own. I did not collaborate with anyone.

Signed: Hall, Tim

Date: 9-17/2020